



Ryerson University Department of Electrical and Computer Engineering COE328 – Digital Systems

Course Number	COE 328
Course Title	Digital Systems
Semester/Year	Fall 2023
Instructor	Arghavan Asad
TA Name	Seham Al Abdul Wahid

Lab/Tutorial Report No.	6
-------------------------	---

Report Title	Design of a Simple General-Purpose Processor
--------------	----------------------------------------------

Section No.	9
Group No.	7
Submission Date	Dec 3, 2023
Due Date	Dec 4, 2023

Table Of Contents:

Introduction:	3
Components:	3
Description of Components:	3
Latch 1/Latch 2:	3
Truth Table:	3
Circuit Diagram / Block Diagram:	3
Waveform:	4
VHDL:	4
4:16 Decoder:	5
Truth Table:	5
Circuit Diagram / Block Diagram:	6
Waveform:	6
VHDL:	7
Mealy FSM:	8
Truth Table:	8
Circuit Diagram / Block Diagram:	9
Waveform:	9
VHDL:	10
SSEG:	14
Truth Table:	14
Circuit Diagram / Block Diagram:	14
Waveform:	14
VHDL:	14
ALU_1:	14
Description:	14
Block Diagram:	14
Table of Microcode:	14
Waveform:	14
VHDL:	16
ALU_2:	16
Description:	16
Block Diagram:	16
Table of Microcode:	16
Waveform:	16
VHDL:	17
ALU_3:	18
Description:	18
Block Diagram:	18
Table of Microcode:	18
Waveform:	18
VHDL:	19
Conclusion:	19

Introduction:

The purpose of the lab is to design and implement a ALU to create a General Purpose Processor. The four key components in creating this device are procuring the input data, a storage unit, a control unit, and the ALU core. The General Purpose Processor consists of , 2 latches, 3 seven segment displays a 4 to 16 decoder, and an FSM (Mealy in this case). The first step is to input two 8 bit binary values, A and B (from the last two numbers of the student ID) into the 2 latches which are a part of the storage unit. The Control unit consists of a 4 to 16 decoder and the mealy machine counter which cycles through the 9 states while the decoder decodes the current state from the FSM to send to the ALU. The ALU takes the 16 bit input from the decoder and does an operation depending on the value from the decoder and returns a 8 bit value. The ALU has 9 different operations which then goes to the SSEGs to display the numbers in hexadecimal.

Components:

Description of Components:

In this lab, there are 5 components that make up the General Purpose Processor. The first component is the latch which takes an 8 bit input and temporarily stores the data to be used by the ALU. The second component is the Mealy machine which counts up from 0 to 8 and outputs the current states into the decoder. The third component is the 4 to 16 decoder which takes the states and outputs the corresponding microcode to the ALU. The fourth component is the ALU which performs the operation corresponding to the microcode and outputs the data to the final component, the SSEG, which takes the output from the ALU and displays it.

Latch 1/Latch 2:

Truth Table:

$$A = (53)_{16} = 01010011 \quad B = (87)_{16} = 10000111$$

Input	Reset		Input	Output (Reset = 0)	Output (Reset = 1)
A	0	1	01010011	00000000	01010011
B	0	1	10000111	00000000	10000111

Truth table for latch 1 and latch 2

Circuit Diagram / Block Diagram:


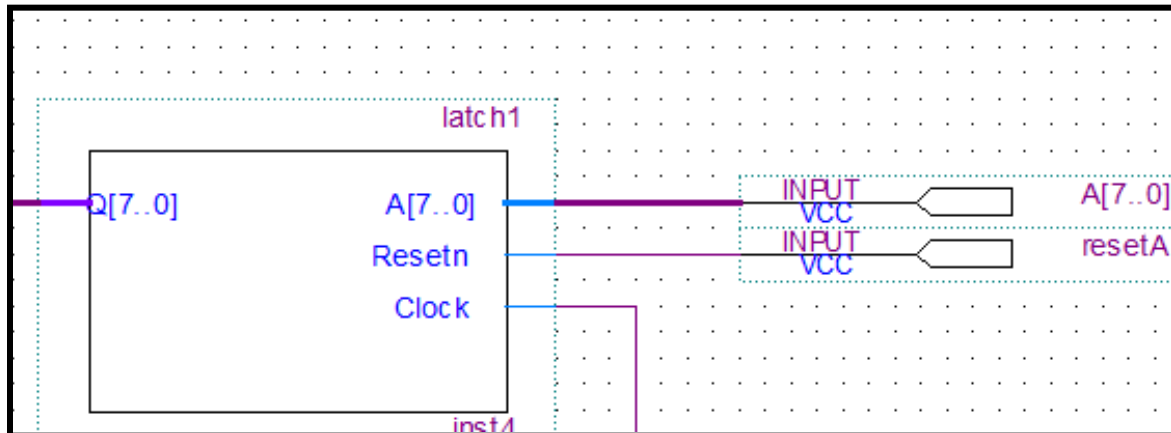


Diagram of Latch 1 (only difference between one and two is that the input is B instead of A)

Waveform:

 

Waveform for one of the latches

VHDL:

```
1  LIBRARY ieee ;
2  USE ieee.std_logic_1164.all;
3  ENTITY latch1 IS
4  PORT (A : IN STD_LOGIC_VECTOR(7 DOWNTO 0) ; -- 8 bit A input
5        Resetn, Clock : IN STD_LOGIC ;-- 1 bit clock input and 1 bit reset input bit
6        Q: OUT STD_LOGIC_VECTOR(7 DOWNTO 0)) ;-- 8 bit output
7  END latch1 ;
8  ARCHITECTURE Behavior OF latch1 IS
9  BEGIN
10 PROCESS ( Resetn, Clock ) -- Process takes reset and clock as inputs
11 BEGIN
12 IF Resetn = '1' THEN -- when reset input is '1' the latches does not operate
13   Q <= "00000000";
14 ELSEIF Clock'EVENT AND Clock = '1' THEN -- level sensitive based on clock
15   Q <= A;
16 END IF;
17 END PROCESS;
18 END Behavior;
19
```

VHDL code for both latches

4:16 Decoder:


Truth Table:

4:16 Decoder Truth Table

En	Input	Output
1	0000	0000000000000001
1	0001	0000000000000010
1	0010	0000000000000100
1	0011	0000000000001000
1	0100	0000000000010000
1	0101	0000000000100000
1	0110	0000000001000000
1	0111	0000000010000000
1	1000	0000000100000000
1	1001	0000001000000000
1	1010	0000010000000000
1	1011	0000100000000000
1	1100	0001000000000000
1	1101	0010000000000000
1	1110	0100000000000000
1	1111	1000000000000000


The decoder only works when enable is 1

Circuit Diagram / Block Diagram:

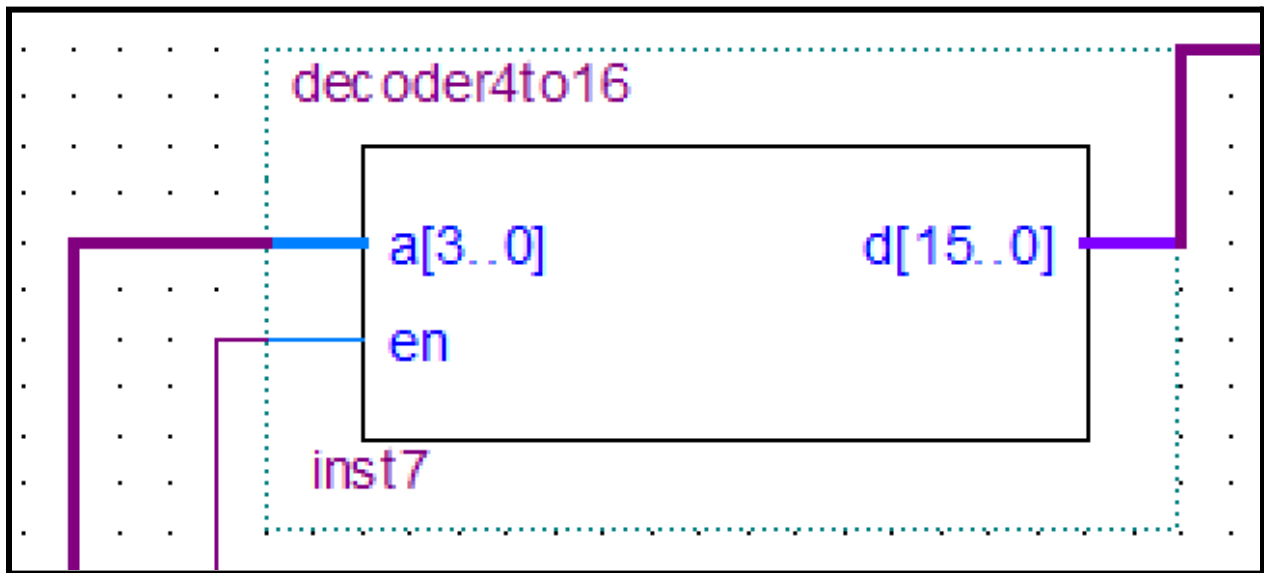

4:16 Decoder block diagram

Waveform:

 

4:16 Decoder waveform

VHDL:

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity decoder4to16 is
4  port (a : in std_logic_vector(3 downto 0);
5        en : in std_logic;
6        d : out std_logic_vector(15 downto 0));
7  end decoder4to16;
8
9  architecture decoder of decoder4to16 is
10 begin
11     process (a)
12     begin
13         if (en = '0') then
14             d <= "0000000000000000";
15         else
16             case a is
17             when "0000" => d <= "0000000000000001";
18             when "0001" => d <= "0000000000000010";
19             when "0010" => d <= "0000000000000100";
20             when "0011" => d <= "0000000000001000";
21             when "0100" => d <= "0000000000010000";
22             when "0101" => d <= "0000000000100000";
23             when "0110" => d <= "0000000001000000";
24             when "0111" => d <= "0000000010000000";
25             when "1000" => d <= "0000000100000000";
26             when "1001" => d <= "0000001000000000";
27             when "1010" => d <= "0000010000000000";
28             when "1011" => d <= "0000100000000000";
29             when "1100" => d <= "0001000000000000";
30             when "1101" => d <= "0010000000000000";
31             when "1110" => d <= "0100000000000000";
32             when "1111" => d <= "1000000000000000";
33             when others => d <= "0000000000000000";
34             end case;
35         end if;
36     end process;
37 end decoder;
```

4:16 Decoder VHDL


Mealy FSM:

Truth Table:

Current State (Decimal)	Current State (Binary)	Student Number (Decimal)	Student Number (Binary)	Next State (Binary)		Student Number Output (Binary)	
				Data_in = 0	Data_in = 1	Data_in =0	Data_in =1
0	0000	5	0101	0000	0001	0101	0111
1	0001	0	0000	0001	0010	0000	0101
2	0010	1	0001	0010	0011	0001	0000
3	0011	1	0001	0011	0100	0001	0001
4	0100	7	0111	0100	0101	0111	0001
5	0101	5	0101	0101	0110	0101	0111
6	0110	3	0011	0110	0111	0011	0101
7	0111	8	1000	0111	1000	1000	0011
8	1000	7	0111	1000	0000	0111	1000


Truth table for Mealy counter. When data in is 0, the state stays the same and the output of the student number is in the same order. When data in is 1, the state moves to the next state and the student number changes accordingly.

Circuit Diagram / Block Diagram:

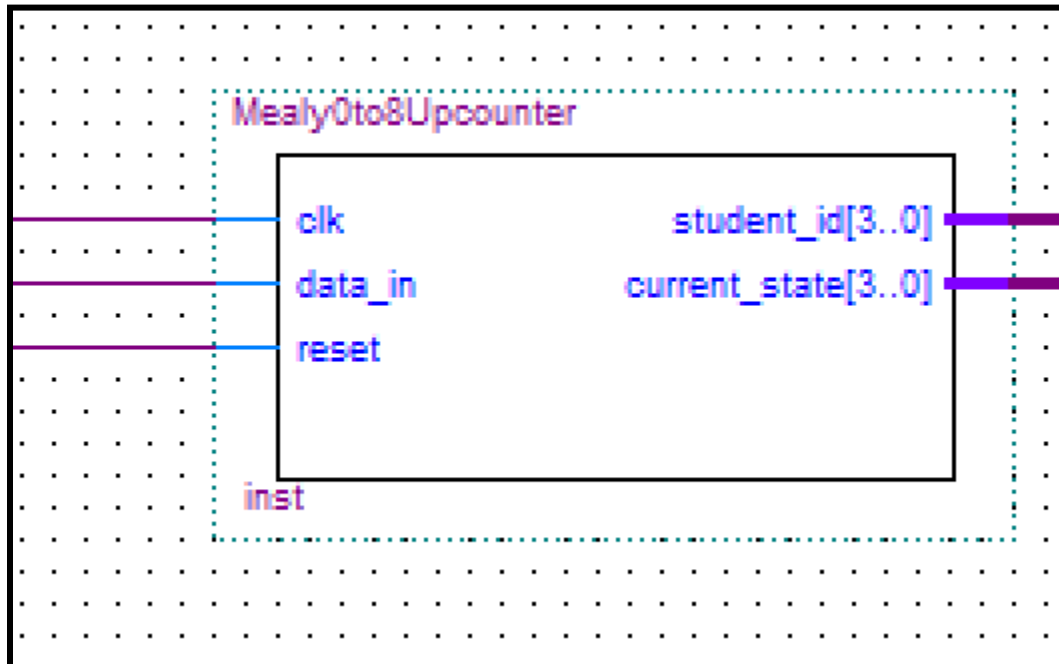

Block diagram for Mealy counter

Waveform:

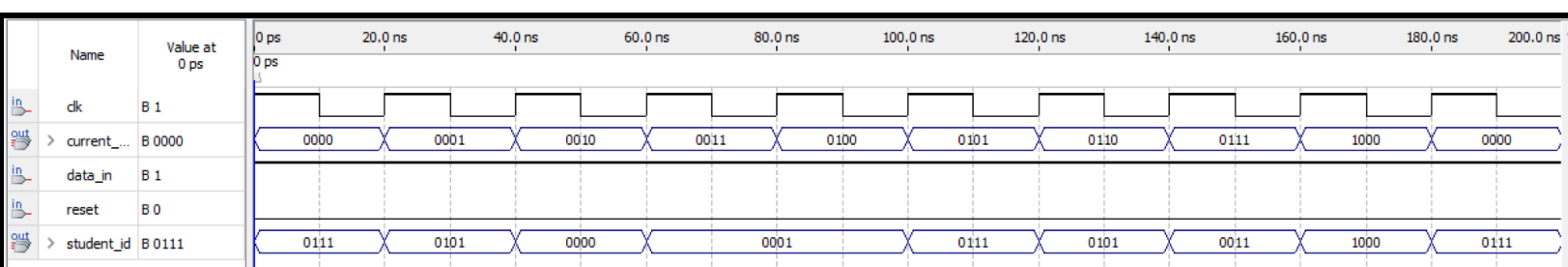

Waveform for Mealy counter when data_in equals 1

VHDL:

```
61      elsif (data_in = '0') then
62          yfsm <= s4;
63      end if;
64
65      when s5 =>
66          if (data_in = '1') then
67              yfsm <= s6;
68          elsif (data_in = '0') then
69              yfsm <= s5;
70          end if;
71
72      when s6 =>
73          if (data_in = '1') then
74              yfsm <= s7;
75          elsif (data_in = '0') then
76              yfsm <= s6;
77          end if;
78
79      when s7 =>
80          if (data_in = '1') then
81              yfsm <= s8;
82          elsif (data_in = '0') then
83              yfsm <= s7;
84          end if;
85
86      when s8 =>
87          if (data_in = '1') then
88              yfsm <= s0;
89          elsif (data_in = '0') then
90              yfsm <= s8;
91          end if;
92
```

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  entity Mealy0to8Upcounter is
4      port
5      (
6          clk: in std_logic;
7          data_in: in std_logic;
8          reset: in std_logic;
9          student_id: out std_logic_vector(3 downto 0);
10         current_state: out std_logic_vector(3 downto 0)
11     );
12 end entity;
13 architecture fsm of Mealy0to8Upcounter is
14
15     type state_type is (s0,s1,s2,s3,s4,s5,s6,s7,s8);
16
17     signal yfsm: state_type;
18
19 begin
20     process (clk,reset)
21     begin
22         if reset = '1' then
23             yfsm <= s0;
24         elsif (clk'EVENT AND clk = '1') then
25
26             case yfsm is --how FSM moves (upcounter, cycling through states 0 to 8 )
27             when s0 =>
28                 if (data_in = '1') then
29                     yfsm <= s1;
30                 elsif (data_in = '0') then
31                     yfsm <= s0;
32                 end if;

```

```

31         yfsm <= s0;
32     end if;
33
34     when s1 =>
35         if (data_in = '1') then
36             yfsm <= s2;
37         elsif (data_in = '0') then
38             yfsm <= s1;
39         end if;
40
41     when s2 =>
42         if (data_in = '1') then
43             yfsm <= s3;
44
45         elsif (data_in = '0')
46         then
47             yfsm <= s2;
48         end if;
49
50     when s3 =>
51         if (data_in = '1') then
52             yfsm <= s4;
53
54         elsif (data_in = '0') then
55             yfsm <= s3;
56         end if;
57
58     when s4 =>
59         if (data_in = '1') then
60             yfsm <= s5;
61         elsif (data_in = '0') then
62             yfsm <= s4;

```

```

94     end case;
95     end if;
96 end process;
97
98 process (yfsm, data_in)
99 begin
100     case yfsm is
101
102         when s0 => --at s0
103             current_state <= "0000"; --default current state
104             if (data_in = '1') then
105                 student_id <= "0111"; --7
106             elsif (data_in = '0') then
107                 student_id <= "0101"; --5
108             end if;
109
110         when s1 => --at s1
111             current_state <= "0001"; --default current state
112             if (data_in = '1') then
113                 student_id <= "0101"; --5
114             elsif (data_in = '0') then
115                 student_id <= "0000"; --0
116             end if;
117
118         when s2 => --at s2
119             current_state <= "0010"; --default current state
120             if (data_in = '1') then
121                 student_id <= "0000"; --0
122             elsif (data_in = '0') then
123                 student_id <= "0001"; --1
124             end if;
125

```

```

124         end if;
125
126         when s3 => --at s3
127             current_state <= "0011"; --default current state
128             if (data_in = '1') then
129                 student_id <= "0001"; --1
130             elsif (data_in = '0') then
131                 student_id <= "0001"; --1
132             end if;
133
134         when s4 => --at s4
135             current_state <= "0100"; --default current state
136             if (data_in = '1') then
137                 student_id <= "0001"; --1
138             elsif (data_in = '0') then
139                 student_id <= "0111"; --7
140             end if;
141
142         when s5 => --at s5
143             current_state <= "0101"; --default current state
144             if (data_in = '1') then
145                 student_id <= "0111"; --3
146             elsif (data_in = '0') then
147                 student_id <= "0101"; --5
148             end if;
149
150         when s6 => --at s6
151             current_state <= "0110"; --default current state
152             if (data_in = '1') then
153                 student_id <= "0101"; --5
154             elsif (data_in = '0') then
155                 student_id <= "0011"; --3

```

```

148         end if;
149
150         when s6 => --at s6
151             current_state <= "0110"; --default current state
152             if (data_in = '1') then
153                 student_id <= "0101"; --5
154             elsif (data_in = '0') then
155                 student_id <= "0011"; --3
156             end if;
157
158         when s7 => --at s7
159             current_state <= "0111"; --default current state
160             if (data_in = '1') then
161                 student_id <= "0011"; --3
162             elsif (data_in = '0') then
163                 student_id <= "1000"; --8
164             end if;
165
166         when s8 => --at s8
167             current_state <= "1000"; --default current state
168             if (data_in = '1') then
169                 student_id <= "1000"; --5
170             elsif (data_in = '0') then
171                 student_id <= "0111"; --7
172             end if;
173     end case;
174
175 end process;
176
177 end fsm;
178

```

VHDL code for Mealy counter

SSEG:

Truth Table:


Input	Output (abcdefg)	Hexadecimal
0000	0000000	0
0001	0110000	1
0010	1101101	2
0011	1111001	3
0100	0110011	4
0101	1011011	5
0110	1011111	6
0111	1110000	7
1000	1111111	8
1001	1110011	9
1010	1110111	A
1011	0011111	B
1100	0001101	C
1101	0111101	D
1110	1001111	E
1111	1000111	F

Truth table for the seven segment display for part 1 and 2


Input	Output (abcdefg)	Y/N
0000	1110110	N
0001	0110011	Y

Truth table for the seven segment display for part 3

Circuit Diagram / Block Diagram:

 


 Block diagram for the seven segment display for part 1 and 2




Block diagram for the seven segment display for part 3

Waveform:

 

 Waveform for SSEG when 1010 or 10 is inputted for part 1 and 2



Waveform for SSEG when 0101 or 5 is inputted for part 3

VHDL:

```
1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY sseg2 IS
5  PORT (negative : IN STD_LOGIC;
6        bcd : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
7        leds, negativeSign: OUT STD_LOGIC_VECTOR(0 TO 6));
8  END sseg2;
9
10 ARCHITECTURE Behavior OF sseg2 IS
11 BEGIN
12     PROCESS (bcd)
13     BEGIN
14         if negative = '1' then
15             negativeSign <= "0000001";
16         else
17             negativeSign <="0000000";
18         END IF;
19
20         CASE bcd IS -- abcdefg
21             WHEN "0000" => leds <= NOT"0000001";
22             WHEN "0001" => leds <= NOT"1001111";
23             WHEN "0010" => leds <= NOT"0010010";
24             WHEN "0011" => leds <= NOT"0000110";
25             WHEN "0100" => leds <= NOT"1001100";
26             WHEN "0101" => leds <= NOT"0100100";
27             WHEN "0110" => leds <= NOT"0100000";
28             WHEN "0111" => leds <= NOT"0001111";
29             WHEN "1000" => leds <= NOT"0000000";
30             WHEN "1001" => leds <= NOT"0001100";
31             WHEN "1010" => leds <= NOT"0001000";
32             WHEN "1011" => leds <= NOT"1100000";
33             WHEN "1100" => leds <= NOT"1110010";
34             WHEN "1101" => leds <= NOT"1000010";
35             WHEN "1110" => leds <= NOT"0110000";
36             WHEN "1111" => leds <= NOT"0111000";
37             WHEN OTHERS => leds <= "-----";
38         END CASE;
39     END PROCESS;
40 END Behavior;
41
42
```

VHDL code for SSEG part 1 and 2

```

1  LIBRARY ieee;
2  USE ieee.std_logic_1164.all;
3
4  ENTITY sseg3 IS
5  PORT (negative : IN STD_LOGIC;
6        bcd : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
7        leds, negativeSign: OUT STD_LOGIC_VECTOR(0 TO 6));
8  END sseg3;
9
10 ARCHITECTURE Behavior OF sseg3 IS
11 BEGIN
12   PROCESS (bcd)
13   BEGIN
14     if negative = '1' then
15       negativeSign <= "1111110";
16     else
17       negativeSign <= "1111111";
18     END if;
19
20     CASE bcd IS -- abcdefg
21     WHEN "0000" => leds <= "1110110"; -- n
22     WHEN "0001" => leds <= "0110011"; -- y
23     WHEN OTHERS => leds <= "-----";
24     END CASE;
25   END PROCESS;
26 END Behavior;
27

```

VHDL code for SSEG part 3


ALU_1:

Description:

The General Purpose Processor (GPP) consists of storage units, a ALU, a control unit and a seven segment display unit. The most important component is the ALU as it does the computation of the imputed values. The up-counting from the FSM passes through the decoder which interprets the microcode and influences the type of operation the ALU performs to the two inputs (A and B) from the two latches. After the operation is complete, the outcome is passed to the two SSEGs which, using LEDs, display the hexadecimal equivalent of the output. The GPP has many inputs and outputs. The first input comes from the user who inputs the last four digits of their student number in binary from hexadecimal. The first two of the four digits are stored into A which holds 8 bits while the last two are stored in B. The two inputs are sent to the latches

which output A and B to the ALU. The Mealy machine cycles through 9 states each corresponding to the student number. The states of the machine are inputted into the decoder which turns the states into microcodes that are passed to the ALU. The ALU reads the microcodes and performs the specific operation to the A and B inputs before outputting to the SSEGs which displays the hexadecimal equivalent of the ALU output. The first SSEG displays the first hexadecimal equivalent, the second displays the last hexadecimal equivalent and the last displays the negative sign if the number is negative. The purpose of the inputs A and B are to be inputs for the arithmetic operations done by the ALU. The control unit outputs the operation that will be performed on the inputs A and B. ALU outputs the final answer which will be inputted to the SSEG to be displayed in hexadecimal format.

Block Diagram:

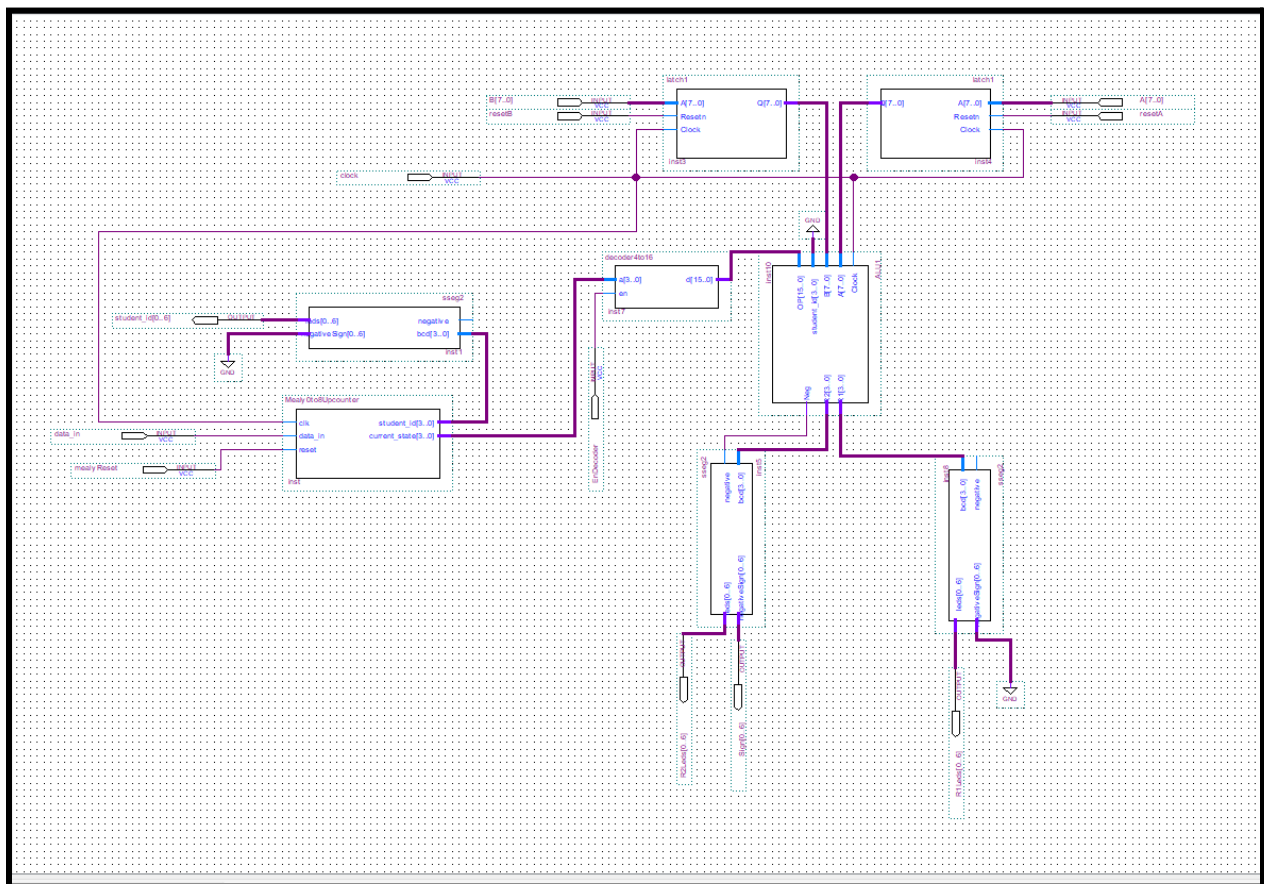

Block diagram of GPP1 and ALU1

Table of Microcode:


Function	Microcode (From Decoder)	Operation
1	0000000000000001	Sum(A,B)
2	0000000000000010	Diff(A,B)
3	0000000000000100	\overline{A}
4	0000000000001000	$\overline{A \cdot B}$
5	0000000000010000	$\overline{A + B}$
6	0000000000100000	$A \cdot B$
7	0000000001000000	$A \oplus B$
8	0000000010000000	$A + B$
9	0000000100000000	$\overline{A \oplus B}$

Table of microcodes for GPP 1 for part 1

Truth Table for Problem Set 1						
Input of Latch1 (A)			Input of Latch2 (B)			
Hexadecimal	53		Hexadecimal	87		
Binary	01010011		Binary	10000111		
ASU1		Result in Binary		abcdefg		
Function #	Operation	Result 2	Result 1	SSEG2	SSEG1	Sign SSEG
1	Sum(A,B)	1101	1010	D: 0111101	A:1110111	0000000
2	Diff(A,B)	0011	0100	3: 1111001	4: 0110011	0000001
3	\overline{A}	1010	1100	A: 1110111	C:0001101	0000000
4	$\overline{A \bullet B}$	1111	1100	F: 1000111	C:0001101	0000000
5	$\overline{A + B}$	0010	1000	2: 1101101	8:1111111	0000000
6	$A \bullet B$	0000	0011	0: 1111110	3: 1111001	0000000
7	$A \oplus B$	1101	0100	D: 0111101	4: 0110011	0000000
8	$A + B$	1101	0111	D: 0111101	7: 1110000	0000000
9	$\overline{A \oplus B}$	0010	1011	2:1101101	B: 0011111	0000000

Truth table for GPP 1

Waveform:

 

ALU1 Waveform running the sum function



GPP1 Waveform (after the red line the numbers are correct)

VHDL:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4  use IEEE.NUMERIC_STD.ALL;
5  entity ALU1 is
6  port( Clock : in std_logic; -- input clock signal
7        A,B : in unsigned(7 downto 0); -- 8-bit inputs from latches A and B
8        student_id : in unsigned(3 downto 0); -- 4 bit student id from FSM
9        OP : in unsigned(15 downto 0); -- 16-bit selector for Operation from Decoder
10       Neg: out std_logic; -- is the result negative ? Set-ve bit output
11       R1 : out unsigned(3 downto 0); -- lower 4-bits of 8-bit Result Output
12       R2 : out unsigned(3 downto 0); -- higher 4-bits of 8-bit Result Output
13   end ALU1;
14   architecture calculation of ALU1 is -- temporary signal declarations.
15   signal Reg1,Reg2,Result : unsigned(7 downto 0) := (others => '0');
16   signal Reg4 : unsigned (0 to 7);
17   begin
18   process(Clock, OP)
19   begin
20   if(rising_edge(Clock)) THEN -- Do the calculation @ positive edge of clock cycle.
21   case OP is
22   WHEN "0000000000000001"=>
23   -- Do Addition for Reg1 and Reg2
24   Result <= Reg1 + Reg2;
25   Neg <= '0';
26   when "0000000000000010" =>

```

```

31   when "0000000000000010" =>
32   if Reg1<Reg2 then
33   Result <= Reg2 - Reg1;
34   neg <= '1';
35   else
36   Result <= Reg1 - Reg2;
37   neg <= '0';
38   end if;
39
40   WHEN "0000000000000100"=>
41   --Do Inverse
42   Result <= NOT Reg1;
43   Neg <= '0';
44
45   WHEN "0000000000001000"=>
46   -- Do Boolean NAND
47   Result <= NOT(Reg1 AND Reg2);
48   Neg <= '0';
49
50   WHEN "0000000000010000"=>
51   -- Do Boolean NOR
52   Result <= NOT(Reg1 OR Reg2);
53   Neg <= '0';
54
55   WHEN "0000000000100000"=>
56   -- Do Boolean AND
57   Result <= Reg1 AND Reg2;
58   Neg <= '0';
59
60   WHEN "0000000001000000"=>
61   -- Do Boolean XOR

```

```

54     Neg <= '0';
55
56     WHEN "0000000000100000"=>
57         -- Do Boolean AND
58         Result <= Reg1 AND Reg2;
59         Neg <= '0';
60
61     WHEN "0000000001000000"=>
62         -- Do Boolean XOR
63         Result <= Reg1 XOR Reg2;
64         Neg <= '0';
65
66     WHEN "0000000010000000"=>
67         -- Do Boolean OR
68         Result <= Reg1 OR Reg2;
69         Neg <= '0';
70
71     WHEN "0000000100000000"=>
72         -- Do Boolean XNOR
73         Result <= Reg1 XNOR Reg2;
74         Neg <= '0';
75
76     WHEN OTHERS =>
77         -- Don't care, do nothing
78     end case;
79 end if;
80 end process;
81 R1 <= Result(3 downto 0); -- Since the output seven segments can
82 R2 <= Result(7 downto 4); -- only 4-bits, split the 8-bit to two 4-bits.
83 end calculation;
84

```

VHDL Code for ALU 1


ALU_2:

(Function g)

Description:

The purpose of the ALU2 is to perform operations that are different to ALU1 based on the function given. The ALU2 is similar to ALU1 as they both perform an operation based on the microcode sent from the decoder. After every rising edge, the Mealy machine outputs a state from 0 to 8 which the decoder reads and sends the equivalent microcode to ALU2 so that it can perform the operation. The only difference between ALU1 and ALU2 is that the operations which are based on the table g, are different for each microcode. ALU2 takes in 2 inputs, A and B from the latches as well as the decoder input to perform the proper operation. The output of the ALU2 is split into two 4 bit representations to be sent to two SSEGs so that they can display the hexadecimal equivalent. The purpose of the inputs A and B are to be inputs for the arithmetic operations done by the ALU. The control unit outputs the operation that will be performed on the

Block Diagram:

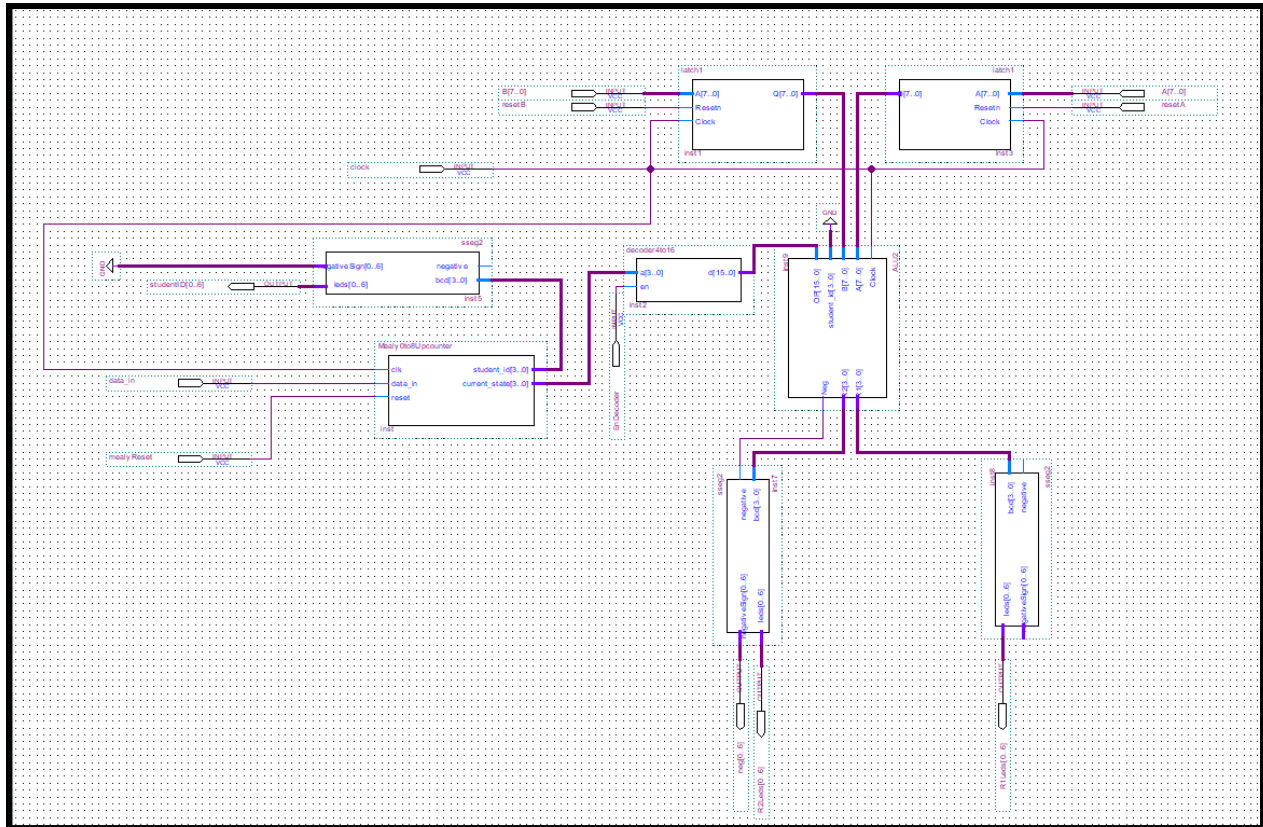

Block diagram of GPP1 and ALU1

Table of Microcode:


Function	Microcode (From Decoder)	Operation
1	0000000000000001	Invert Sig-bit A
2	0000000000000010	SHL A by 4, all 1 after
3	0000000000000100	Invert Upper 4-bit B
4	0000000000001000	Min(A, B)
5	0000000000010000	Sum(A,B) add 4
6	0000000000100000	A add 3
7	0000000001000000	Even-bits A = Even-bits B
8	0000000010000000	$\overline{A \oplus B}$
9	0000000100000000	ROR B by 3 bits

Table of microcodes for GPP 1 for part 1


Truth Table for Problem Set 2					
Input of Latch1 (A)			Input of Latch2 (B)		
Hexadecimal	01		Hexadecimal	38	
Binary	00000001		Binary	00111000	
ASU2		Result in Binary		abcdefg	
Function #	Operation	Result 2	Result 1	SSEG2	SSEG1
1	Invert Sig-bit A	1100	1010	C:0001101	A:1110111
2	SHL A by 4, all 1 after	0011	1111	3:1111001	F:1000111
3	Invert Upper 4-bit B	0111	0111	7:1110000	7:1110000
4	Min(A, B)	0101	0011	5:1011011	3:1111001
5	Sum(A,B) add 4	1101	1110	D:0111101	E:1001111
6	A add 3	0101	0110	5:1011011	6:1011111
7	Even-bits A = Even-bits B	0000	0111	0:1111110	7:1110000
8	$\overline{A \oplus B}$	0010	1011	2:1101101	B:0011111
9	ROR B by 3 bits	1111	0000	F:1000111	0:0000000

Truth table for GPP2

Waveform:

 

 Waveform for ALU2 inverting the bit significance of A (operation 1)



Waveform for GPP 2 (after the red line the numbers are correct)

VHDL:

```

1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3  use IEEE.STD_LOGIC_UNSIGNED.ALL;
4  use IEEE.NUMERIC_STD.ALL;
5  entity ALU2 is
6  port( Clock : in std_logic; -- input clock signal
7        A,B : in unsigned(7 downto 0); -- 8-bit inputs from latches A and B
8        student_id : in unsigned(3 downto 0); -- 4 bit student id from FSM
9        OP : in unsigned(15 downto 0); -- 16-bit selector for Operation from Decoder
10       Neg: out std_logic; -- is the result negative ? Set-ve bit output
11       R1 : out unsigned(3 downto 0); -- lower 4-bits of 8-bit Result Output
12       R2 : out unsigned(3 downto 0)); -- higher 4-bits of 8-bit Result Output
13  end ALU2;
14  architecture calculation of ALU2 is -- temporary signal declarations.
15  signal Reg1,Reg2,Result : unsigned(7 downto 0) := (others => '0');
16  signal Reg4 : unsigned (0 to 7);
17  begin
18  Reg1 <= A; -- temporarily store A in Reg1 local variable
19  Reg2 <= B; -- temporarily store B in Reg2 local variable
20  process(Clock, OP)
21  begin
22  if(rising_edge(Clock)) THEN -- Do the calculation @ positive edge of clock cycle.
23  case OP is
24  WHEN "0000000000000001" =>
25      Result(0)<= Reg1(7);
26      Result(1)<= Reg1(6);
27      Result(2)<= Reg1(5);
28      Result(3)<= Reg1(4);
29      Result(4)<= Reg1(3);
30      Result(5)<= Reg1(2);
31      Result(6)<= Reg1(1);
32      Result(7)<= Reg1(0);
33      --Neg<='0';
34
35  WHEN "0000000000000010" =>
36
37      Result<= Reg1 sll 4;
38      Result(0)<='1';
39      Result(1)<='1';
40      Result(2)<='1';
41      Result(3)<='1';
42
43  WHEN "0000000000000100" =>
44      Result(7)<= Not Reg2(7);
45      Result(6)<= Not Reg2(6);
46      Result(5)<= Not Reg2(5);
47      Result(4)<= Not Reg2(4);
48      Result(3)<= Reg2(3);
49      Result(2)<= Reg2(2);
50  end case;
51  end if;
52  end process;
53  end architecture;

```

```

44     WHEN "0000000000000100" =>
45         Result(7) <= Not Reg2(7);
46         Result(6) <= Not Reg2(6);
47         Result(5) <= Not Reg2(5);
48         Result(4) <= Not Reg2(4);
49         Result(3) <= Reg2(3);
50         Result(2) <= Reg2(2);
51         Result(1) <= Reg2(1);
52         Result(0) <= Reg2(0);
53
54
55     WHEN "0000000000001000" =>
56         if (Reg1 <= Reg2) then
57             Result <= Reg1;
58         else
59             Result <= Reg2;
60         end if;
61
62     WHEN "0000000000010000" => Result <= Reg1 + Reg2 + "00000100"; --note before was 4
63
64     WHEN "0000000000100000" => Result <= Reg1 + "00000011";
65
66     WHEN "0000000001000000" =>
67
68         Result(0) <= Reg2(0);
69         Result(1) <= Reg1(1);
70         Result(2) <= Reg2(2);
71         Result(3) <= Reg1(3);
72         Result(4) <= Reg2(4);
73         Result(5) <= Reg1(5);
74         Result(6) <= Reg2(6);
75         Result(7) <= Reg1(7);
76
77
78     WHEN "0000000010000000" => Result <= (Reg1 XNOR Reg2);
79
80     WHEN "0000000100000000" => Result <= Reg2 ROR 3;
81
82     WHEN OTHERS =>
83         Result <= "-----";
84
85
86     end case;
87 end if;
88 end process;
89 R1 <= Result(3 downto 0); -- Since the output seven segments can
90 R2 <= Result(7 downto 4); -- only 4-bits, split the 8-bit to two 4-bits.
91 end calculation;
92

```


VHDL code for ALU 2

ALU_3:

Description:

The purpose of ALU3 is to compare one of the 2 digits of A, in this case (53)₁₆, with each number of the student ID. If the student ID number matches either 5 or 3 in binary, the SSEG will display a “y” otherwise it will display a “n”. The rising edge of the clock allows the Mealy machine to cycle through all the states of the student number and ALU3 compares the two numbers. Once the ALU3 is finished comparing the numbers, it will output either “00000000” or “00000001” to the SSEG which interprets “00000000” as “n” and “00000001” as “y”. The SSEG then displays this output. The purpose of the input A is that it allows the ALU3 to compare it with the student number. The control unit outputs the operation that will be performed on the input A. The ALU3 output is the result of the operation done by the ALU3 which is imputed to the SSEG. The purpose of the SSEG is to display “y” or “n” according to if the numbers match.

Block Diagram:

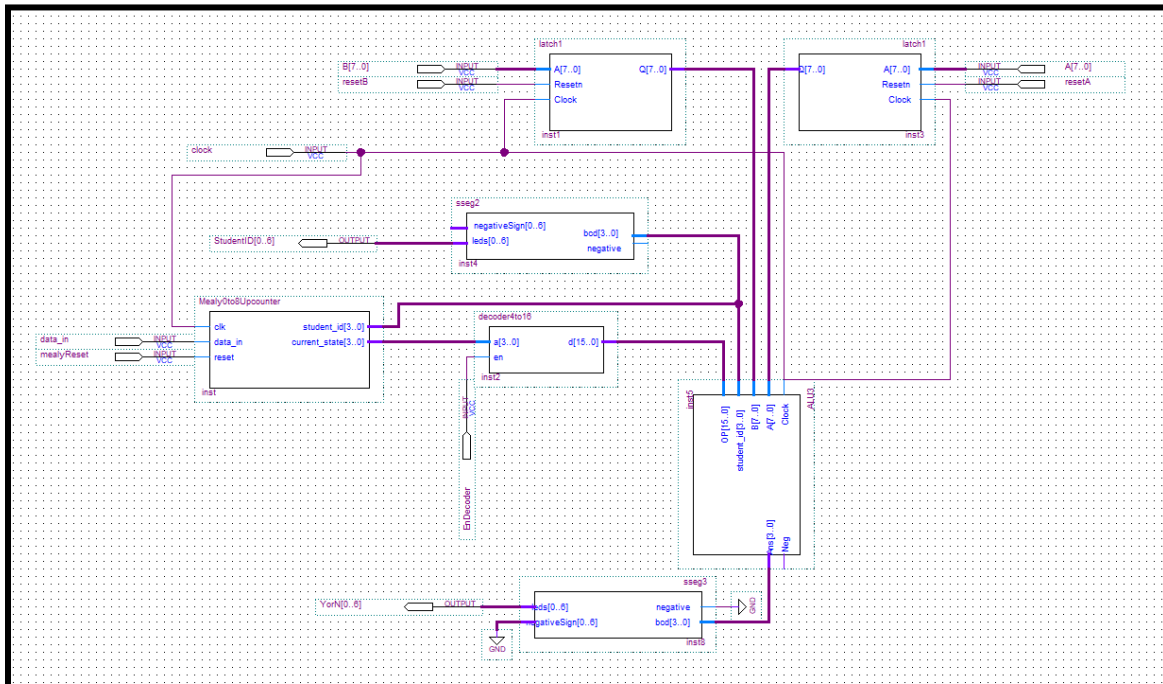

Block diagram for GPP3 and ALU3

Table of Microcode:


Function	Microcode (From Decoder)	Operation
1	0000000000000001	Compare the first number of student number with both bits of A in hexadecimal
2	0000000000000010	Compare the second number of student number with both bits of A in hexadecimal
3	0000000000000100	Compare the third number of student number with both bits of A in hexadecimal
4	0000000000001000	Compare the fourth number of student number with both bits of A in hexadecimal
5	0000000000010000	Compare the fifth number of student number with both bits of A in hexadecimal
6	0000000000100000	Compare the sixth number of student number with both bits of A in hexadecimal
7	0000000001000000	Compare the seventh number of student number with both bits of A in hexadecimal
8	0000000010000000	Compare the eighth number of student number with both bits of A in hexadecimal
9	0000000100000000	Compare the ninth number of student number with both bits of A in hexadecimal

Table of microcode for GPP3


Truth Table for Problem Set 3						
Input of Latch1 (A)						
Hexadecimal			53			
Binary			01010011			
ASU3		A in Binary		Output in Binary	SSEG	
Function #	Student ID	First 4-bits	Last 4-bits		abcdefg	Y or N
1	5: 0101	0101	0011	0001	0110011	Y
2	0: 0000	0101	0011	0000	1110110	N
3	1: 0001	0101	0011	0000	1110110	N
4	1: 0001	0101	0011	0000	1110110	N
5	7: 0111	0101	0011	0000	1110110	N
6	5: 0101	0101	0011	0001	0110011	Y
7	3: 0011	0101	0011	0001	0110011	Y
8	8: 1000	0101	0011	0000	1110110	N
9	7: 0111	0101	0011	0000	1110110	N

Truth table for GPP3

Waveform:

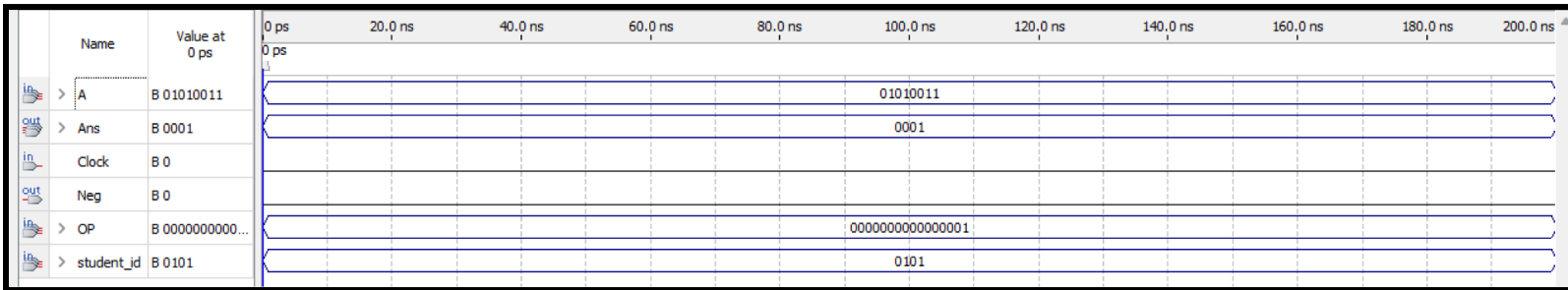

 Waveform for ALU3 testing if 5 (0101) is equal to one of the two bits of A (01010011)



Waveform for GPP3 (after the red line the numbers are correct)

VHDL:

```

1  LIBRARY IEEE;
2  USE IEEE.STD_LOGIC_1164.all;
3  USE IEEE.STD_LOGIC_UNSIGNED.all;
4  USE IEEE.NUMERIC_STD.all;
5  ENTITY ALU3 IS
6  PORT (Clock: IN STD_LOGIC;
7        A: IN UNSIGNED(7 DOWNTO 0);
8        student_id: IN UNSIGNED(3 DOWNTO 0);
9        OP: IN UNSIGNED(15 DOWNTO 0);
10       Neg: OUT STD_LOGIC;
11       Ans: OUT UNSIGNED(3 DOWNTO 0));
12
13  END ALU3;
14
15  ARCHITECTURE calculation OF ALU3 IS
16  SIGNAL Reg1, Reg2, Result: UNSIGNED(7 DOWNTO 0) := (OTHERS => '0');
17  SIGNAL Reg4: UNSIGNED (0 TO 7);
18  BEGIN
19
20     Reg1 <= A;
21
22  PROCESS(Clock, OP)
23  BEGIN
24  CASE OP IS
25      WHEN "0000000000000001" =>
26          if (Reg1(3 downto 0) = student_id) then
27              Result <= "00000001";
28          elsif (Reg1(7 downto 4) = student_id) then
29              Result <= "00000001";
30          else
31              Result <= "00000000";
32          end if;
33
34      WHEN "0000000000000010" =>
35          if (Reg1(3 downto 0) = student_id) then
36              Result <= "00000001";
37          elsif (Reg1(7 downto 4) = student_id) then
38              Result <= "00000001";
39          else
40              Result <= "00000000";
41          end if;
42
43      WHEN "0000000000000100" =>
44          if (Reg1(3 downto 0) = student_id) then
45              Result <= "00000001";
46          elsif (Reg1(7 downto 4) = student_id) then
47              Result <= "00000001";
48          else
49              Result <= "00000000";
50          end if;
51
52      WHEN "0000000000001000" =>
53          if (Reg1(3 downto 0) = student_id) then
54              Result <= "00000001";
55          elsif (Reg1(7 downto 4) = student_id) then
56              Result <= "00000001";
57          else
58              Result <= "00000000";
59          end if;
60
61      WHEN "0000000000010000" =>
62          if (Reg1(3 downto 0) = student_id) then
63              Result <= "00000001";
64          elsif (Reg1(7 downto 4) = student_id) then
65              Result <= "00000001";
66          else
67              Result <= "00000000";
68          end if;
69
70      WHEN "0000000000100000" =>
71          if (Reg1(3 downto 0) = student_id) then
72              Result <= "00000001";
73          elsif (Reg1(7 downto 4) = student_id) then
74              Result <= "00000001";
75          else
76              Result <= "00000000";
77          end if;
78
79      WHEN "0000000001000000" =>
80          if (Reg1(3 downto 0) = student_id) then
81              Result <= "00000001";
82          elsif (Reg1(7 downto 4) = student_id) then
83              Result <= "00000001";
84          else
85              Result <= "00000000";
86          end if;
87
88      WHEN "0000000010000000" =>
89          if (Reg1(3 downto 0) = student_id) then
90              Result <= "00000001";
91          elsif (Reg1(7 downto 4) = student_id) then
92              Result <= "00000001";
93          else
94              Result <= "00000000";
95          end if;
96
97      WHEN "0000000100000000" =>
98          if (Reg1(3 downto 0) = student_id) then
99              Result <= "00000001";
100         elsif (Reg1(7 downto 4) = student_id) then
101             Result <= "00000001";
102         else
103             Result <= "00000000";
104         end if;
105
106      WHEN "0000001000000000" =>
107          if (Reg1(3 downto 0) = student_id) then
108              Result <= "00000001";
109          elsif (Reg1(7 downto 4) = student_id) then
110              Result <= "00000001";
111          else
112              Result <= "00000000";
113          end if;
114
115      WHEN "0000010000000000" =>
116          if (Reg1(3 downto 0) = student_id) then
117              Result <= "00000001";
118          elsif (Reg1(7 downto 4) = student_id) then
119              Result <= "00000001";
120          else
121              Result <= "00000000";
122          end if;
123
124      WHEN "0000100000000000" =>
125          if (Reg1(3 downto 0) = student_id) then
126              Result <= "00000001";
127          elsif (Reg1(7 downto 4) = student_id) then
128              Result <= "00000001";
129          else
130              Result <= "00000000";
131          end if;
132
133      WHEN "0001000000000000" =>
134          if (Reg1(3 downto 0) = student_id) then
135              Result <= "00000001";
136          elsif (Reg1(7 downto 4) = student_id) then
137              Result <= "00000001";
138          else
139              Result <= "00000000";
140          end if;
141
142      WHEN "0010000000000000" =>
143          if (Reg1(3 downto 0) = student_id) then
144              Result <= "00000001";
145          elsif (Reg1(7 downto 4) = student_id) then
146              Result <= "00000001";
147          else
148              Result <= "00000000";
149          end if;
150
151      WHEN "0100000000000000" =>
152          if (Reg1(3 downto 0) = student_id) then
153              Result <= "00000001";
154          elsif (Reg1(7 downto 4) = student_id) then
155              Result <= "00000001";
156          else
157              Result <= "00000000";
158          end if;
159
160      WHEN "1000000000000000" =>
161          if (Reg1(3 downto 0) = student_id) then
162              Result <= "00000001";
163          elsif (Reg1(7 downto 4) = student_id) then
164              Result <= "00000001";
165          else
166              Result <= "00000000";
167          end if;
168
169      WHEN "0000000000000000" =>
170          Result <= "00000000";
171      end case;
172  end PROCESS;
173
174  Neg <= '0';
175  Ans <= Result;
176
177  end calculation OF ALU3;

```

```

67  else
68      Result <= "00000000";
69  end if;
70
71  WHEN "00000000001000000" =>
72  if (Reg1(3 downto 0) = student_id) then
73      Result <= "00000001";
74  elsif (Reg1(7 downto 4) = student_id) then
75      Result <= "00000001";
76  else
77      Result <= "00000000";
78  end if;
79
80  WHEN "00000000001000000" =>
81  if (Reg1(3 downto 0) = student_id) then
82      Result <= "00000001";
83  elsif (Reg1(7 downto 4) = student_id) then
84      Result <= "00000001";
85  else
86      Result <= "00000000";
87  end if;
88
89  WHEN "00000000010000000" =>
90  if (Reg1(3 downto 0) = student_id) then
91      Result <= "00000001";
92  elsif (Reg1(7 downto 4) = student_id) then
93      Result <= "00000001";
94  else
95      Result <= "00000000";
96  end if;
97
98  WHEN "00000000100000000" =>
99  if (Reg1(3 downto 0) = student_id) then
100      Result <= "00000001";
101  elsif (Reg1(7 downto 4) = student_id) then
102      Result <= "00000001";
103  else
104      Result <= "00000000";
105  end if;
106
107  WHEN OTHERS =>
108      Result <= "-----";
109
110  END CASE;
111  END PROCESS;
112
113  Ans <= Result(3 downto 0);
114
115  END calculation;

```

Conclusion:

In conclusion, in lab 6 we successfully created multiple GPPs by implementing 3 different ALUs and different components created from all the labs throughout the semester like the mealy machine, 4 to 16 decoder, SSEG, and the latches. Through the waveforms, we were able to confirm that ALU1, ALU2, and ALU3 were working properly and that when connected to create each GPP for the different problem sets, they outputted the correct waveform. Each ALU consists of a mealy machine that would cycle through the different states which allowed the ALUs to perform different operations with the two inputs A and B. The importance of each component was emphasized in this lab as many problems we faced were due to small errors in a specific component. The completion of lab 6 demonstrates the growth in the semester from being new to quartus to creating our own GPP.